

# AN14190

OPAMP usage on MCXN947

Rev. 1.0 — 20 January 2024

Application note

## Document information

Information	Content
Keywords	AN14190, OPAMP, motor control, power management, amplify
Abstract	This application note describes the functions of OPAMP module and how to use OPAMP features on MCXN947.



## 1 Introduction to MCX OPAMP

OPAMP is widely used in motor control, power management applications, which can be used for current and voltage detection, small signal amplifiers, and so on. The MCXN947 microcontroller integrates three individual OPAMP modules. The OPAMP module in MCXN947 can be configured to Low Noise mode or High-Speed mode. Both positive and negative gains are programmable. In addition, both positive and negative gains can be configured to the Buffer mode so that the user can connect external resistors to configure the gains and functions. The MCXN947 OPAMP module provides two positive input pins. The trigger controller can switch these two pins. In addition, the OPAMP positive reference voltage, negative gain resistor, ladder voltage output, and OPAMP output can be connected to ADC. The positive reference voltage can be connected to VDDA2/2, DAC, VERF0, and VERF1V internally. [Figure 1](#) shows the MCX N947 OPAMP module block diagram.

This application note describes the functions of OPAMP module and how to use OPAMP features on MCXN947.

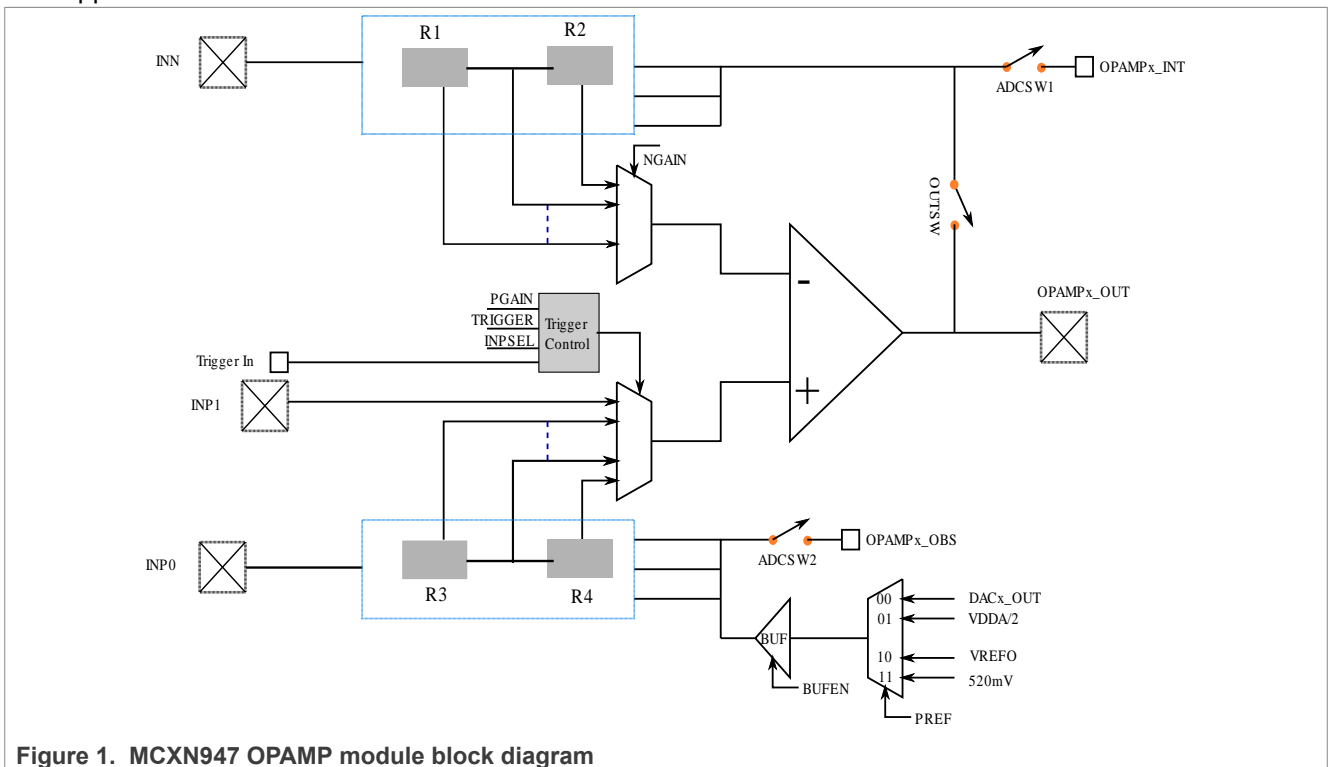


Figure 1. MCXN947 OPAMP module block diagram


## 2 Typical kinds of OPAMP

OPAMP is an electronic integrated circuit, which contains a multistage amplifier circuit. Its input stage is a differential amplifier circuit. It has high input resistance and the ability to suppress zero drift.

An ideal OPAMP contains the following characteristics:


- Input bias current  $I_B = 0$
- Input offset voltage  $V_E = 0$
- Input impedance  $Z_{IN} = \infty$
- Output impedance  $Z_{OUT} = 0$
- Gain  $a = \infty$

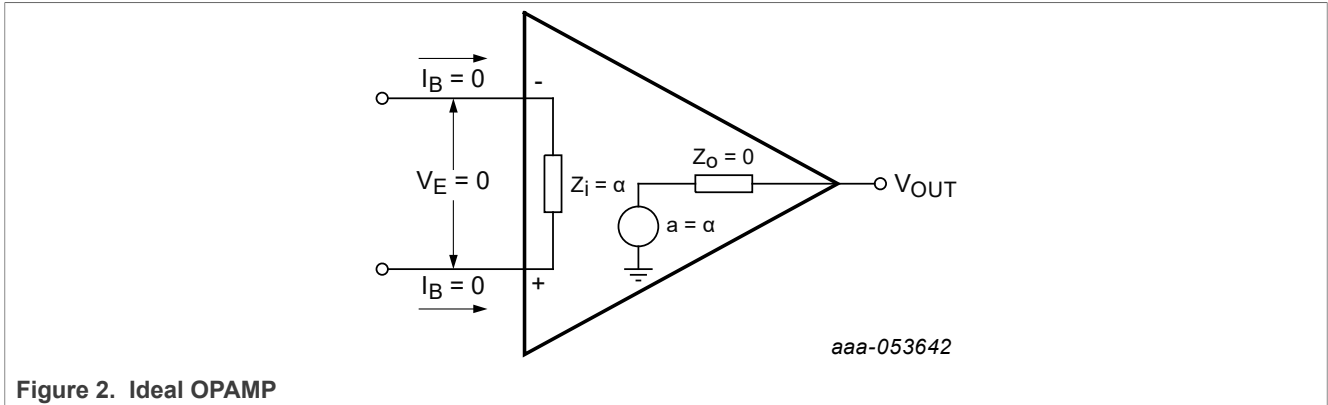To simplify the analysis, see [Figure 2](#) for an ideal OPAMP.



### 2.1 Voltage follower OPAMP

Figure 3 shows the connection of the voltage follower OPAMP.

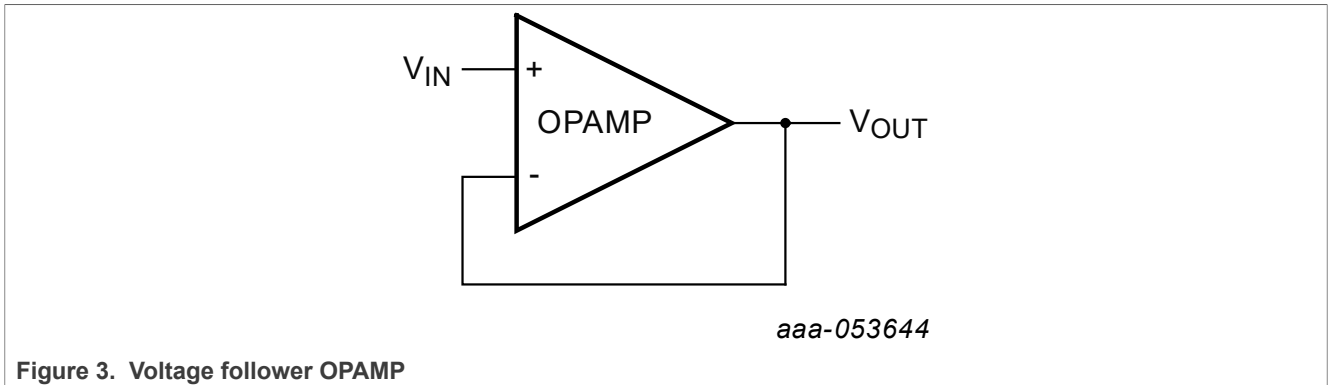

In the non-inverting OPAMP, if let the  $R_2 = 0$  and remove  $R_1$ , we can get the equation (1) as below:

$$V_{OUT} = V_{IN} \tag{1}$$

To perform impedance adaptation on input signals, the circuit uses OPAMP as a follower buffer.

### 2.2 Non-inverting OPAMP

Figure 4 shows the non-inverting OPAMP connection.

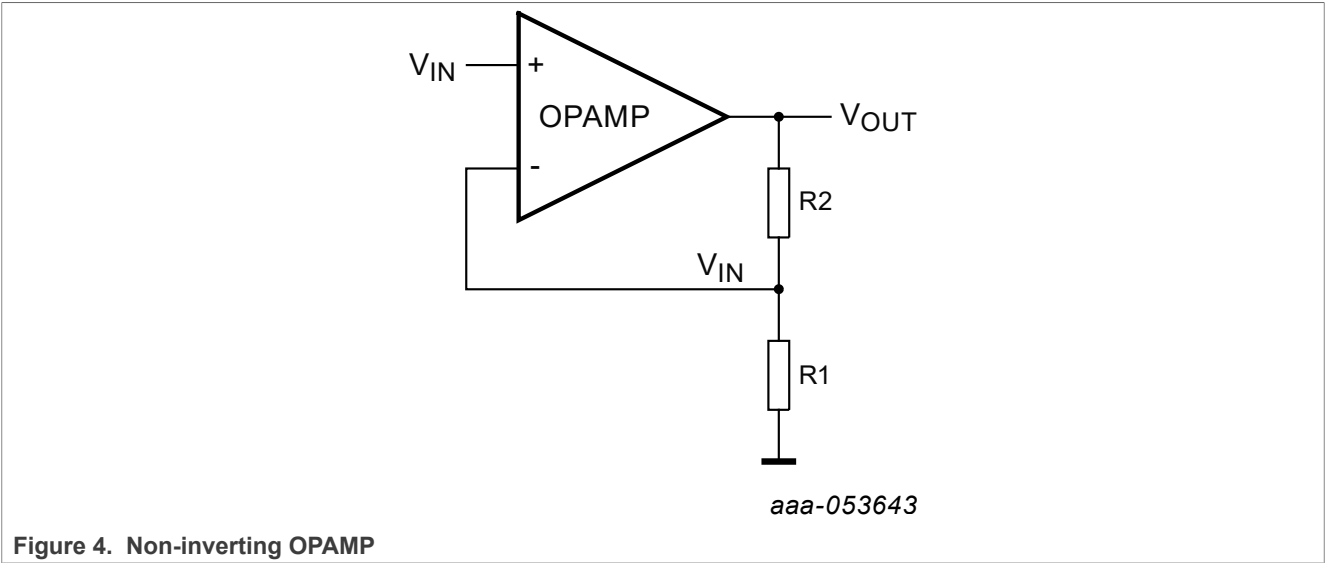


Figure 4. Non-inverting OPAMP

Non-inverting OPAMP has the input signal connected to its positive input. According to the ideal OPAMP assumptions, when input current  $I_B = 0$  and input offset voltage  $V_E = 0$ , we get the equation as below:

$$V_{IN} = V_{OUT} \frac{R_1}{R_1 + R_2} \tag{2}$$

Then:

$$V_{OUT} = V_{IN} \left( 1 + \frac{R_2}{R_1} \right) \tag{3}$$

The output signal is the amplified signal and non-inverted from the input signal. The circuit input impedance is an infinite impedance.

### 2.3 Inverting OPAMP

Figure 5 shows the inverting OPAMP connection.

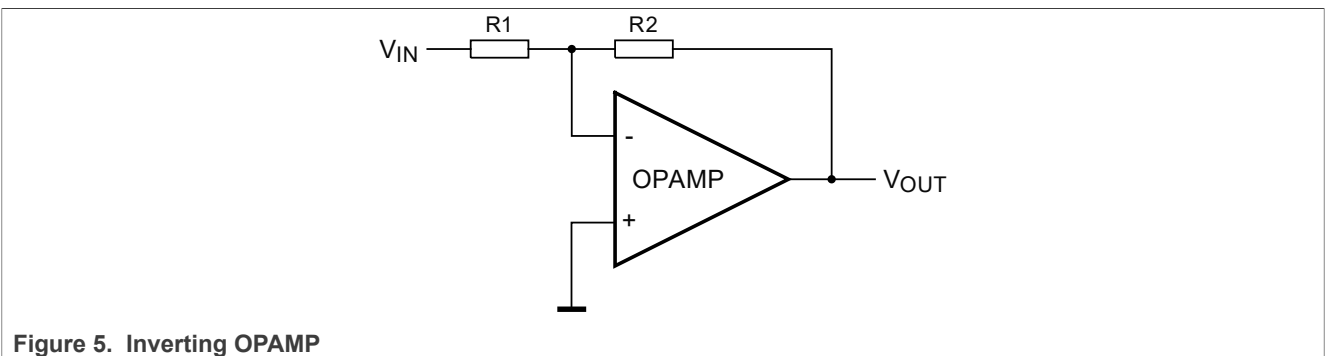


Figure 5. Inverting OPAMP

Inverting OPAMP has the input signal connected to its negative input. According to the ideal OPAMP assumptions, if input current  $I_B = 0$  and input offset voltage  $V_E = 0$ , we get the equation as below:

$$\frac{V_{IN}}{R_1} = - \frac{V_{OUT}}{R_2} \tag{4}$$

Then:

$$V_{OUT} = \left(-\frac{R_2}{R_1}\right)V_{IN} \tag{5}$$

The output signal is the amplified signal and inverted from the input signal.

### 2.4 Differential OPAMP

Figure 6 shows the differential OPAMP connection.

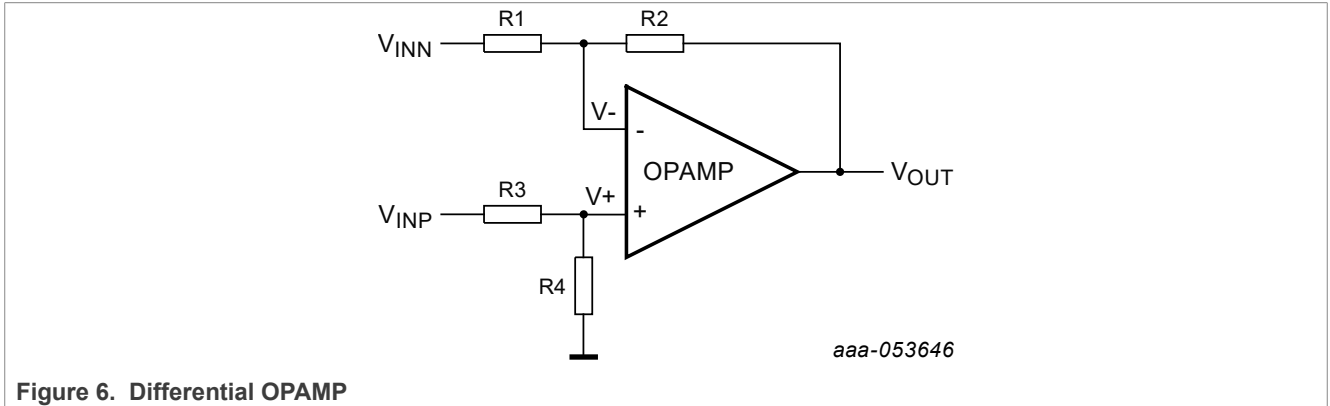


Figure 6. Differential OPAMP

Differential OPAMP amplifies the voltage difference between input signals. According to the ideal OPAMP assumptions, if input current  $I_B = 0$  and input offset voltage  $V_E = 0$ , we get the equation as below:

From:

$$\frac{V_{INP} - V_+}{R_3} = \frac{V_+}{R_4} \tag{6}$$

We can get:

$$V_+ = \frac{R_4}{R_3 + R_4} V_{INP} \tag{7}$$

From:

$$\frac{V_- - V_{INN}}{R_1} = \frac{V_{OUT} - V_-}{R_2} \tag{8}$$

We can get:

$$V_{OUT} = \frac{R_1 + R_2}{R_1} V_- - \frac{R_2}{R_1} V_{INN} \tag{9}$$

According to  $V_+ = V_-$ , from Equation 7 and Equation 9, we can get:

$$V_{OUT} = \frac{R_1 + R_2}{R_1} * \frac{R_4}{R_3 + R_4} V_{INP} - \frac{R_2}{R_1} V_{INN} \tag{10}$$

If  $R_1 = R_3$ ,  $R_2 = R_4$ , then:

$$V_{OUT} = \frac{R_2}{R_1} (V_{INP} - V_{INN}) \tag{11}$$

In the circuit, the differential signal,  $(V_{INP} - V_{INN})$ , is multiplied by the stage gain. The circuit is a differential amplifier. It amplifies only the differential portion of the input signal and rejects the common mode portion of the input signal.

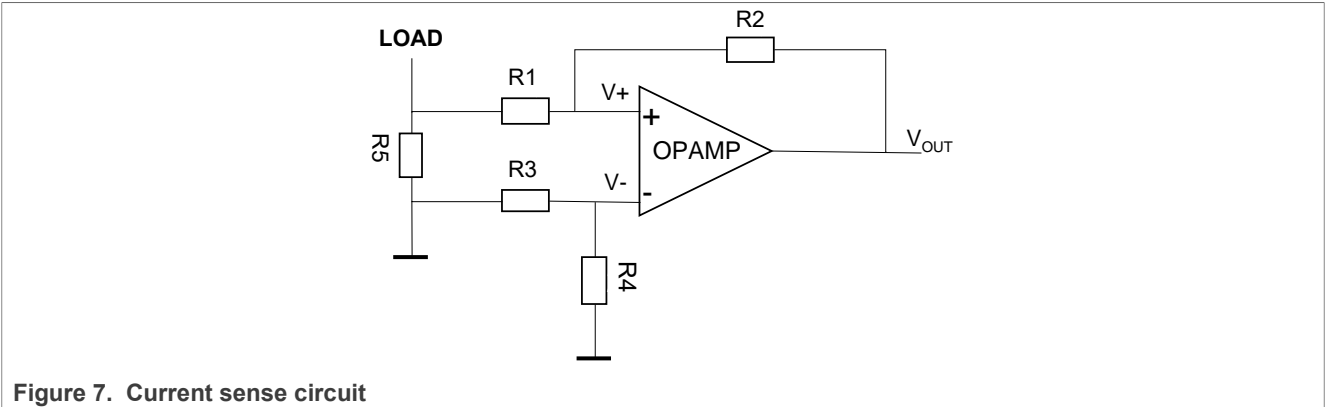


Figure 7. Current sense circuit

Figure 7 shows the differential OPAMP use case. It can be used to detect and calculate the load current.

### 2.5 OPAMP integral circuit

Figure 8 shows the OPAMP to be used in an integral circuit.

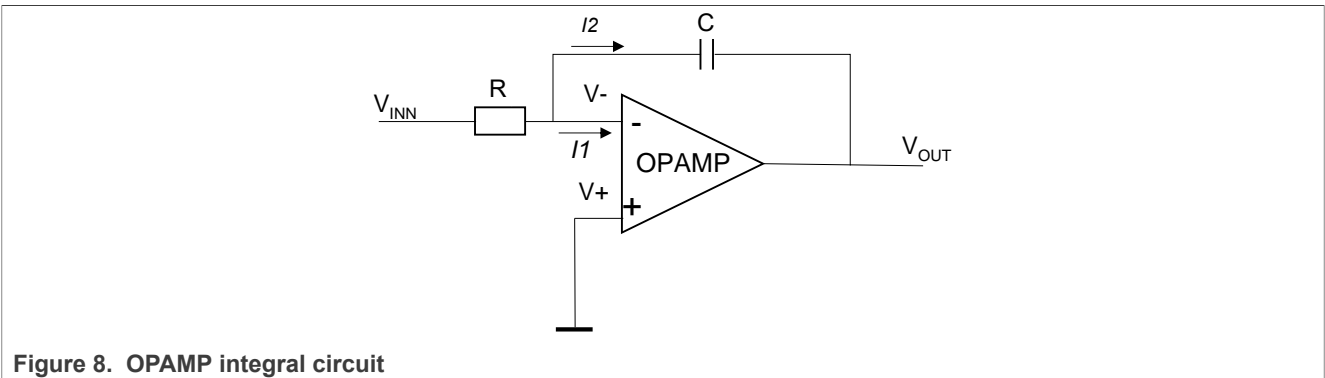


Figure 8. OPAMP integral circuit

Based on the virtual short circuit and virtual open circuit principle as shown in equation (12) and (13):

$$V_+ = V_- \tag{12}$$

$$I_1 = 0 \tag{13}$$

We get equation (14), as below:

$$I_2 = I_1 = \frac{V_{INN}}{R} \tag{14}$$

Assume that the initial voltage of the capacitor is zero, we get equation (15):

$$V_- - V_{OUT} = \frac{1}{C} \int I_2 dt = \frac{1}{C} \int \frac{V_{INN}}{R} dt \tag{15}$$

The equation (16) shows the  $V_{OUT}$  value in an OPAMP out pin:

$$V_{OUT} = - \frac{1}{RC} \int V_{INN} dt \tag{16}$$

### 2.6 OPAMP differentiating circuit

Figure 9 shows the OPAMP to be used in a differential circuit.

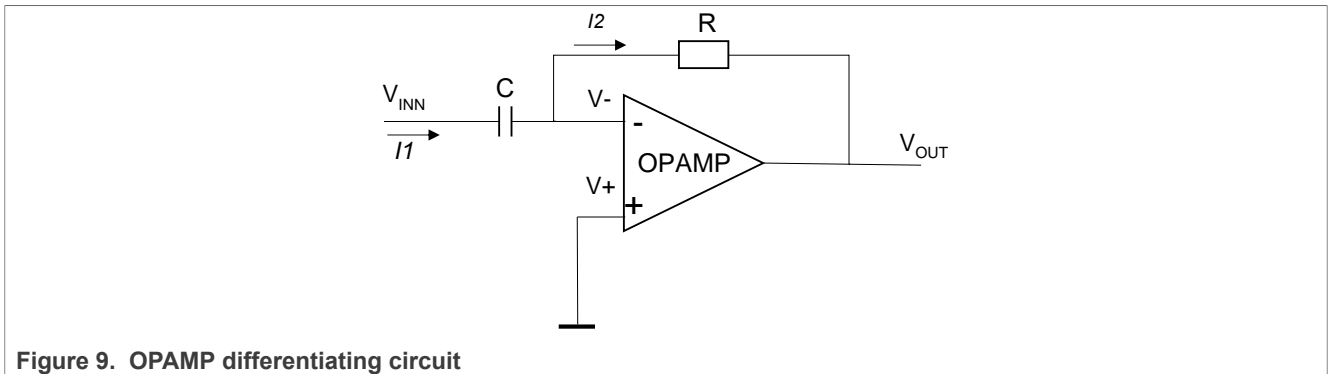


Figure 9. OPAMP differentiating circuit

Based on the virtual short circuit and virtual open circuit principle, we get equation:

$$V_{OUT} = -I_2 * R = -I_1 * R = -RC \frac{dV_{INN}}{dt} \quad (17)$$

The equation (18) shows the  $V_{OUT}$  value in OPAMP out pin:

$$V_{OUT} = -RC \frac{dV_{INN}}{dt} \quad (18)$$

### 3 Demo for OPAMP on MCXN947

In this section, we use FRDM-MCXN947 board to do OPAMP function test and the test demo based on SDK\_2\_14\_0\_FRDM-MCXN947.

#### 3.1 Demo platform

This section describes the hardware and software requirements.

##### 3.1.1 Hardware

The demo is developed on the FRDM-MCXN947 board. [Figure 10](#) shows the MCXN947 FRDM board.



Figure 10. FRDM-MCXN947 board

### 3.1.2 Software

- Software: SDK\_2\_14\_0\_FRDM-MCXN947
- IDE: MDK5.37

## 4 OPAMP module test

The OPAMP module has several functions, such as voltage follower, non-inverting, inverting, differential, and so on. This section introduces how to set up OPAMP functions.



### 4.1 Follower test

Figure 11 shows the follower test hardware settings. To test this function, connect J1-4 with J4-1 on MCXN947-FRDM board. To connect DAC0\_OUT with OPAMP0\_INP0, measure the J8-20 voltage from OPAMP0\_OUT pin.

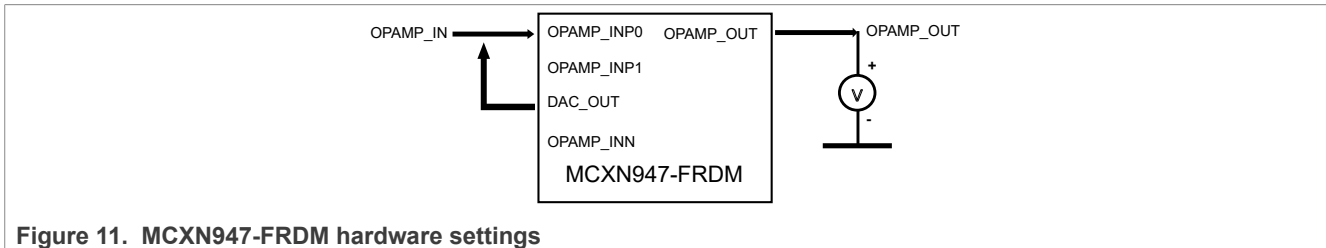


Figure 11. MCXN947-FRDM hardware settings

The following code shows the voltage follower OPAMP test code.

```
void OPAMP_Configuration(void)
{
    opamp_config_t config;
    OPAMP_GetDefaultConfig(&config);
    config.PosInputChannelSelection = kOPAMP_PosInputChannel0;
    config.posGain = kOPAMP_PosGainNonInvert2X;
    config.negGain = kOPAMP_NegGainBufferMode;
    config.enable = true;
    config.enableRefBuffer = false;
    OPAMP_Init(DEMO_OPAMP_BASEADDR, &config);
}
```

### 4.2 Non-inverting test

The hardware settings is same as shown in Figure 11. Connect J1-4 with J4-1 on FRDM-MCXN947 board. To connect DAC0\_OUT with OPAMP0\_INP0, measure the J8-20 voltage from OPAMP0\_OUT pin.

The following code shows the non-inverting OPAMP test code.

```
void OPAMP_Configuration(void)
{
    opamp_config_t config;
    OPAMP_GetDefaultConfig(&config);
    config.PosInputChannelSelection = kOPAMP_PosInputChannel0;
    config.posGain = kOPAMP_PosGainNonInvertDisableBuffer2X;
    config.negGain = kOPAMP_NegGainInvert1X;
    config.enable = true;
    config.enableRefBuffer = false;
    OPAMP_Init(DEMO_OPAMP_BASEADDR, &config);
}
```

### 4.3 Differential test

The hardware settings is same as shown in Figure 11. Connect J1-4 with J4-1 on MCXN947-FRDM board. To connect DAC0\_OUT with OPAMP0\_INP0, measure the J8-20 voltage from OPAMP0\_OUT pin.

The following code shows the differential OPAMP test code.

```
void OPAMP_Configuration(void)
{
    opamp_config_t config;
```

```

OPAMP_GetDefaultConfig(&config);
config.PosInputChannelSelection = kOPAMP_PosInputChannel0;
config.posGain = kOPAMP_PosGainNonInvert1X;
config.negGain = kOPAMP_NegGainInvert1X;
config.posRefVoltage = kOPAMP_PosRefVoltVrefh3;
config.enable = true;
config.enableRefBuffer = true;
OPAMP_Init(DEMO_OPAMP_BASEADDR, &config);
}

```

## 5 Note about the source code in the document

Example code shown in this document has the following copyright and BSD-3-Clause license:

Copyright 2024 NXP Redistribution and use in source and binary forms, with or without modification, are permitted provided that the following conditions are met:

1. Redistributions of source code must retain the above copyright notice, this list of conditions and the following disclaimer.
2. Redistributions in binary form must reproduce the above copyright notice, this list of conditions and the following disclaimer in the documentation and/or other materials must be provided with the distribution.
3. Neither the name of the copyright holder nor the names of its contributors may be used to endorse or promote products derived from this software without specific prior written permission.

THIS SOFTWARE IS PROVIDED BY THE COPYRIGHT HOLDERS AND CONTRIBUTORS "AS IS" AND ANY EXPRESS OR IMPLIED WARRANTIES, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE ARE DISCLAIMED. IN NO EVENT SHALL THE COPYRIGHT HOLDER OR CONTRIBUTORS BE LIABLE FOR ANY DIRECT, INDIRECT, INCIDENTAL, SPECIAL, EXEMPLARY, OR CONSEQUENTIAL DAMAGES (INCLUDING, BUT NOT LIMITED TO, PROCUREMENT OF SUBSTITUTE GOODS OR SERVICES; LOSS OF USE, DATA, OR PROFITS; OR BUSINESS INTERRUPTION) HOWEVER CAUSED AND ON ANY THEORY OF LIABILITY, WHETHER IN CONTRACT, STRICT LIABILITY, OR TORT (INCLUDING NEGLIGENCE OR OTHERWISE) ARISING IN ANY WAY OUT OF THE USE OF THIS SOFTWARE, EVEN IF ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

## 6 Revision history

[Table 1](#) summarizes the revisions done to this document.

**Table 1. Revision history**

Document ID	Release date	Description
AN14190 v.1.0	20 January 2024	Initial public release

## Legal information

### Definitions

**Draft** — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

### Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Terms and conditions of commercial sale** — NXP Semiconductors products are sold subject to the general terms and conditions of commercial sale, as published at <https://www.nxp.com/profile/terms>, unless otherwise agreed in a valid written individual agreement. In case an individual agreement is concluded only the terms and conditions of the respective agreement shall apply. NXP Semiconductors hereby expressly objects to applying the customer's general terms and conditions with regard to the purchase of NXP Semiconductors products by customer.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Suitability for use in non-automotive qualified products** — Unless this document expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

**Translations** — A non-English (translated) version of a document, including the legal information in that document, is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

**Security** — Customer understands that all NXP products may be subject to unidentified vulnerabilities or may support established security standards or specifications with known limitations. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately. Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP.

NXP has a Product Security Incident Response Team (PSIRT) (reachable at [PSIRT@nxp.com](mailto:PSIRT@nxp.com)) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

**NXP B.V.** — NXP B.V. is not an operating company and it does not distribute or sell products.

### Trademarks

Notice: All referenced brands, product names, service names, and trademarks are the property of their respective owners.

**NXP** — wordmark and logo are trademarks of NXP B.V.

**MCM** — is a trademark of NXP B.V.

---

## Contents

---

<b>1</b>	<b>Introduction to MCX OPAMP .....</b>	<b>2</b>
<b>2</b>	<b>Typical kinds of OPAMP .....</b>	<b>2</b>
2.1	Voltage follower OPAMP .....	3
2.2	Non-inverting OPAMP .....	3
2.3	Inverting OPAMP .....	4
2.4	Differential OPAMP .....	5
2.5	OPAMP integral circuit .....	6
2.6	OPAMP differentiating circuit .....	6
<b>3</b>	<b>Demo for OPAMP on MCXN947 .....</b>	<b>7</b>
3.1	Demo platform .....	7
3.1.1	Hardware .....	7
3.1.2	Software .....	8
<b>4</b>	<b>OPAMP module test .....</b>	<b>8</b>
4.1	Follower test .....	9
4.2	Non-inverting test .....	9
4.3	Differential test .....	9
<b>5</b>	<b>Note about the source code in the document .....</b>	<b>10</b>
<b>6</b>	<b>Revision history .....</b>	<b>10</b>
	<b>Legal information .....</b>	<b>11</b>

---

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

---