# AN14236

# NTAG X DNA - Antenna design guide Rev. 1.0 — 27 May 2025

**Application note** 

#### **Document information**

Information	Content
Keywords	Contactless, NTAG X DNA, ISO/IEC 14443, resonance, coil, inlay, antenna, card coil design
Abstract	This document provides guidance for engineers designing magnetic loop antenna coils for NTAG X DNA.



NTAG X DNA - Antenna design guide

#### 1 Introduction

NTAG X DNA can be powered by a magnetic field generated by the PCD. To get the magnetic flux cut by the PICC, it also requires a loop antenna.

This document provides guidance for engineers designing such a magnetic loop antenna coil for NTAG X DNA.

The detailed loop antenna design is explained in <u>ref.[1]</u>. Although such antennas are relatively straightforward in principle and look very similar when comparing various contactless smartcards, experience proves that their parameters do have a noticeable impact on performance.

Note: In this document, the term "NTAG X DNA card" refers to a NTAG X DNA IC-based contactless card.

#### 1.1 How to use this document

This document is covers the hints and notes specific to NTAG X DNA. All the basics and design details are explained in <u>ref.[1]</u>. Use <u>ref.[1]</u> as the base document and apply the notes mentioned in this documents where applicable.

NTAG X DNA - Antenna design guide

## 2 Card coil design notes for NTAG X DNA


There are different classes of antennas widely used in contactless applications for the NTAG X DNA PICC. The design of PICC coils differs for the antenna classic in use. Different application requirements can also lead to differences in antenna design.

The most important parameters for card coil design are:

- · coil area
- · coil quality factor
- the resonance frequency of the transponder under loaded conditions
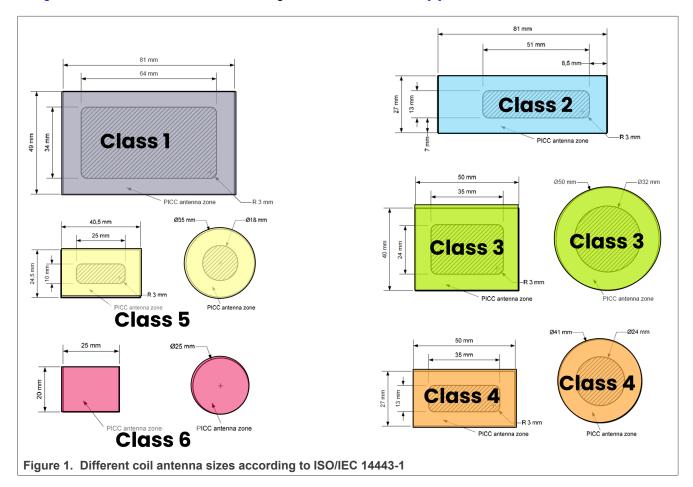
#### 2.1 Different classes of antenna according to ISO/IEC 14443-1

In Figure 1, different antenna sizes according to ISO/IEC 14443-1 ref.[3] are shown.



#### 2.2 Card coil area

Make the card coil area as large as possible. Bending corners are better than sharp corners.

#### 2.3 Coil Q-factor

To get optimum performance and to cover manufacturing tolerances, for NTAG X DNA, the recommended coil Q values are provided in <u>Table 1</u>.

AN14236

All information provided in this document is subject to legal disclaimers.

© 2025 NXP B.V. All rights reserved.

NTAG X DNA - Antenna design guide

#### 2.3.1 Measurement of coil Q-factor

There are different ways to measure the Q-factor of the coil, which may lead to different results. Follow the instructions in <u>ref.[1]</u> or contact your NXP technical support for more information.

#### 2.4 Definition for "loaded" and "unloaded" conditions

"loaded conditions", or just "loaded", means that the NTAG X DNA IC gets enough power to be able to fully operate.

"unloaded conditions", or just "unloaded", means that the NTAG X DNA IC does not get enough power in order to even start to operate.

#### 2.5 Loaded resonance frequency of the transponder

The loaded resonance frequency of the transponder is the resulting resonance frequency, if the IC is operated under loaded conditions.

In general, the appropriate resonance frequency of the transponder depends on the card ICs and applications. To get optimum performance and to cover manufacturing tolerances, the recommended loaded resonance frequency for NTAG X DNA is given in <u>Table 1</u>.

#### 2.5.1 Measurement of loaded resonance frequency of the transponder

There are different ways to measure the resonance frequency of the transponder, which may end up with different results. Follow the instructions in <u>ref.[1]</u> or contact your NXP technical support for more information.

NTAG X DNA - Antenna design guide

## 2.6 NXP recommendation for PICC coil design

Table 1 summarizes the recommendations for PICC coil design.

#### 17 pF chip version:

- NTAG X DNA works properly between 14.5 MHz 16 MHz loaded f<sub>R</sub>. However, for optimization of speed at a 1.5 A/m field strength, a loaded f<sub>R</sub> of 14.5 MHz - 15 MHz is most ideal and recommended.
- For maximum operating distance, the loaded f<sub>R</sub> is ideally close to 14.5 MHz.
- A loaded f<sub>R</sub> too close at 13.56 MHz (e.g 14 MHz) might have an impact on detuning of the reader antenna and might cause reading issues on some reader models.

#### 50 pF chip version:

• NTAG X DNA works best between 13.9 MHz - 14.4 MHz loaded f<sub>R</sub>.

Table 1. PICC coil design recommendation

Antenna class	Recommended chip of NTAG X DNA	Recommended loaded transponder resonance frequency (f <sub>R</sub> )	Recommended Coil Q	Comments
Class 1	17 pF	14.5 MHz < f <sub>R</sub> < 16 MHz		Transponder optimum loaded resonance frequency for stacked 2 cards operation is close to 15 MHz.
Class 2, 3, 4, 5, 6	50 pF	13.9 MHz < f <sub>R</sub> < 14.4 MHz	> 40	For 106 kbit/s and single card application. The optimum loaded resonance frequency is slightly above 13.9 MHz.

Those recommended quality factor values for the Coil are important to ensure good power transfer and to increase the so-called power range of the transponder. Those recommended values will also remain valid for higher bit rates than 106 kbit/s (up to 848 kbit/s).

For CLASS 1 antennas (17 pF IC version), a minimum Coil Q-Factor = 30 is recommended. The resulting transponder Q-factor under "unloaded" conditions is similar to this value. Once the IC starts to operate, the transponder (loaded) Q-Factor is decreasing and this is leading to a loaded Q-Factor in the range of Q = 8-9. This value is a good compromise in the middle of the Range Q = 6-15, which results in a good performance for all data transfer rates (from 106 kbit/s to 848 kbit/s).

All those considerations are also valid for CLASS 2 to CLASS 6 antennas (50 pF IC version), the only difference is that a minimum Coil Q-Factor = 40 is recommended.

Refer to <u>Section 2.9.1</u> in this document for further reference on this topic.

**Note:** Increasing the communication bit rate may reduce the communication distance especially for the small antennas (smaller than class 1).

NTAG X DNA - Antenna design guide


## 2.7 Practical design hints and recommendations for the 17 pF chip version

#### 2.7.1 ID1-sized antennas


Within the confines of the application and the card manufacturing processes used, try to maximize the antenna size. The outermost turn of the antenna coil should be placed as close as possible to the edge of the card represented by an 81 x 49 mm rectangle. Class 1 antenna examples (with two different parameters) are shown in Figure 2.

**Note:** International standards and industry specifications may restrict the choice of the maximum allowed antenna coil size.

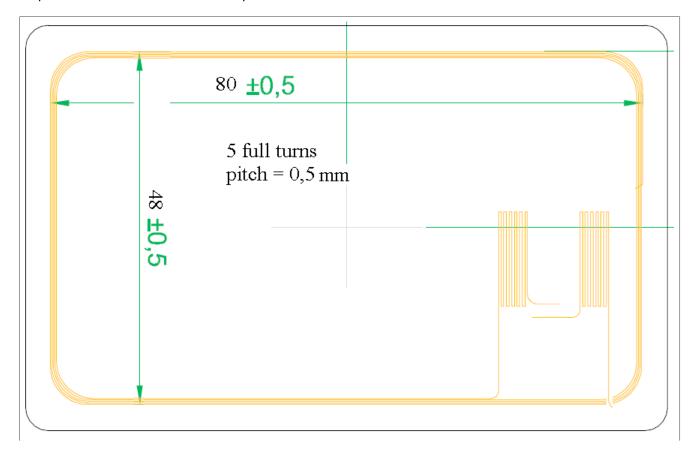For ID1 size (class 1) antenna, the 17 pF chip version is recommended. For all other classes, the usage of the 50 pF version of the NTAG X DNA chip is recommended.



NTAG X DNA - Antenna design guide

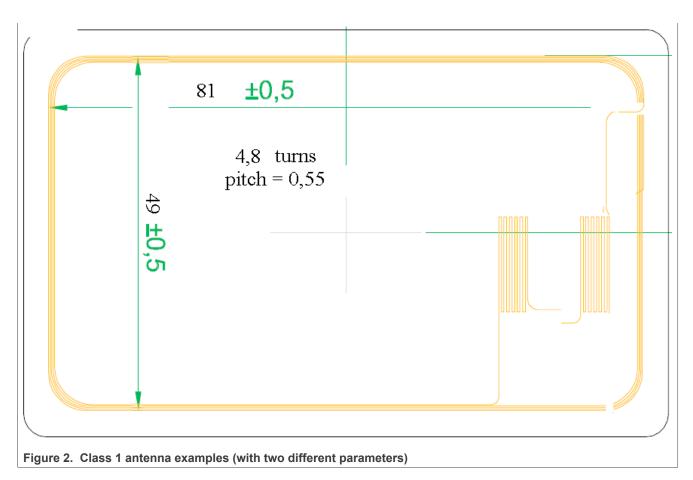

<u>Figure 3</u> shows further examples of typical parameters for different ID1-sized antenna designs. Besides geometrical coil parameters (orange colored area), also measured (blue colored area) and calculated (green colored area) electrical parameters are listed in comparison.

S			Embed	ded Wire	e rectangul	ar Antenna	s	
ioi	outline	mm	72,6 x 42	80,2 x 48	80 x 47,5	80 x 48	80,5 x 48	
ens	wire diam.	mm	0,112	0,112	0,112	0,112	0,112 ?	
Dimensions	wire pitch	mm	0,14	0,45	0,45	0,45	0,3	
٥								
	turns		5	5	4,9	5	5	
묫	Ls @ 1MHz	μН	4,83	4,89	4,69	4,90	5,23	
measured	Rs Q 1 MHz	Ohm	2,05	2,29	2,22	2,24	2,37	
eas	fres	MHz	36,84	38,45	42,58	39,46	39,19	
Ε	Rp @ fres	kOhm	55,00	69,00	90,00	90,00	55,00	
-	Q@fres		63,00	66,00	72,00	70,00		
ate								
퍨	Ср	pF	3,87	3,51	2,98	3,32	3,16	
Calculated	Rs	Ohm	3,92	3,78	3,22	3,38	4,49	
	Q		105,03	110,11	124,00	123,70	99,16	

Figure 3. Typical parameters of different class 1 card antennas


NTAG X DNA - Antenna design guide

## 2.8 Practical design hints and recommendations for the 50 pF chip version

For class 2 and up to class 6 antennas, it is recommended to use the 50 pF chip version.
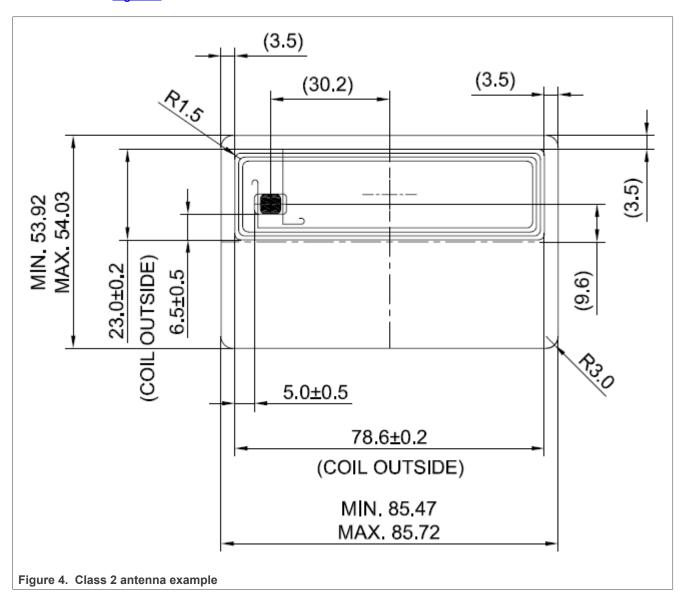
#### 2.8.1 ID ½ sized (class 2) antenna

Geometrical parameters of one possible class 2 size antenna design, as well as its location within the ID1 card area is shown in Figure 4.



NTAG X DNA - Antenna design guide


## 2.9 Antenna coil design considerations for unloaded and loaded conditions (17 pF IC)

#### 2.9.1 Quality factor and bandwidth of the transponder

The quality factor of a transponder  $Q_T$  is an important parameter defined at air interface. The value of  $Q_T$  has to be properly chosen in order to guarantee sufficient performance for both power and data transmission.

The quality factor of the transponder results from the quality factor values of its' both components, the antenna  $(Q_A)$  and the chip  $(Q_C)$ , and is dictated by the component with lower Q-factor, in this case by the  $Q_C$ . Taking into account that both chip electrical parameters (capacitance  $C_C$  and resistance  $R_C$ ) are power-dependent, it is obvious that the  $Q_T$  also changes with power and frequency. This point is relevant when considering  $Q_T$  under "loaded" and "unloaded" conditions.

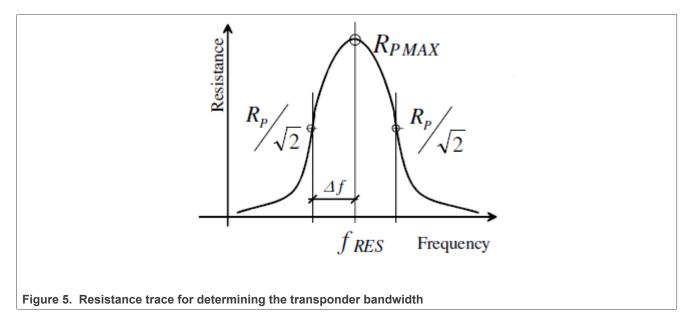For a transponder resonant LCR circuit,  $Q_T$  can be determined in frequency domain.  $Q_T$  is related to the bandwidth, which can be measured from the resistance trace as shown in Figure 5 (see ref.[2]).



 $Q_T$  can be calculated by using Equation 1, which connects three relevant parameters (quality factor  $Q_T$ , resonance frequency  $f_{res}$  and bandwidth B) with each other:

$$Q_T = \frac{f_{res}}{2 \cdot \Delta f} = \frac{f_{res}}{B} \tag{1}$$

Where  $f_{res}$  is a transponder resonance frequency and  $\Delta f$  is defined as in Figure 5.

**Note:** This is only valid, if the broadband equivalent circuit representation really is a parallel resonant circuit.


NTAG X DNA - Antenna design guide

## 2.10 Required transponder bandwidth for (PICC → PCD) data transfer

The demand for data transfer sets certain requirements on the transponder bandwidth B, which limits the transponder quality factor  $Q_T$ . The needed bandwidth is related to the modulation scheme, coding and data rates, used.

The highest data rate, which is defined in the standard, requires the largest transponder bandwidth.

Figure 6 demonstrates how this bandwidth can be calculated for 424 bit/s data rate.

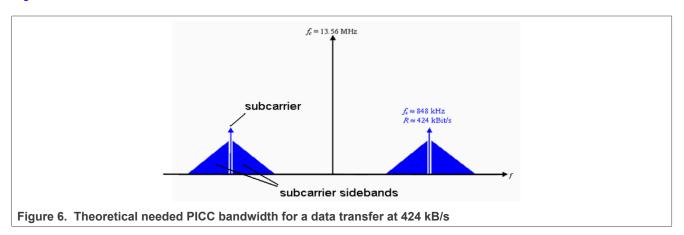

Other possible data rates and their relationship to their associated required bandwidth is given in Table 2.

Table 2. Theoretical PICC needed bandwidth for a data transfer with different data rates

Data rates [kbit/s]	B [MHz]
106	1.8
212	1.9
424	2.1
848	2.5

One important remark: If a transponder bandwidth is smaller, than theoretically required bandwidth, this does not automatically mean that the communication will not be possible. What will happen is that the sideband levels of the card answer will be more damped than 3 dB, (which was accepted for a bandwidth definition), but are still sufficient for successful communication.

**Note:** For higher antenna classes (class 2 to class 6): With coil size reduction the inductance of the coil decreases. Additionally, there is a recommendation to utilize 50 pF IC version together with antennas smaller than class 1. This results in the increase of the transponder  $Q_T$  factor. It is recommended to control resulting  $Q_T$  or bandwidth B of the new designed small transponder, to enable successful communication for all desired data rates.

NTAG X DNA - Antenna design guide

## 3 Terms and abbreviations

#### Table 3. Abbreviations

Acronym	Description
CCDG	Card coil design guide
PCD	Proximity coupling device
PICC	Proximity IC card
f <sub>R</sub> / fres	Resonance frequency

NTAG X DNA - Antenna design guide

## 4 References

- [1] Application note AN11276 NTAG Antenna Design Guide (link)
- [2] M. Gebhart, Air Interface, Antennas and Signals in Contactless Near-Field Communication 2nd lecture in Selected Topics of Advanced Analog Chip Design, 439.224
- [3] Standard ISO/IEC 14443-1 Identification cards Contactless integrated circuit cards Proximity cards Part 1: Physical characteristics

NTAG X DNA - Antenna design guide

## 5 Revision history

#### Table 4. Revision history

Revision	Release date	Description
AN14236 v.1.0	27 May 2025	Initial version

#### NTAG X DNA - Antenna design guide

## **Legal information**

#### **Definitions**

**Draft** — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

#### **Disclaimers**

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Terms and conditions of commercial sale — NXP Semiconductors products are sold subject to the general terms and conditions of commercial sale, as published at https://www.nxp.com/profile/terms, unless otherwise agreed in a valid written individual agreement. In case an individual agreement is concluded only the terms and conditions of the respective agreement shall apply. NXP Semiconductors hereby expressly objects to applying the customer's general terms and conditions with regard to the purchase of NXP Semiconductors products by customer.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Suitability for use in non-automotive qualified products — Unless this document expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

**HTML publications** — An HTML version, if available, of this document is provided as a courtesy. Definitive information is contained in the applicable document in PDF format. If there is a discrepancy between the HTML document and the PDF document, the PDF document has priority.

**Translations** — A non-English (translated) version of a document, including the legal information in that document, is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Security — Customer understands that all NXP products may be subject to unidentified vulnerabilities or may support established security standards or specifications with known limitations. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately. Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP.

NXP has a Product Security Incident Response Team (PSIRT) (reachable at <a href="PSIRT@nxp.com">PSIRT@nxp.com</a>) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

**NXP B.V.** — NXP B.V. is not an operating company and it does not distribute or sell products.

#### **Trademarks**

Notice: All referenced brands, product names, service names, and trademarks are the property of their respective owners.

NXP — wordmark and logo are trademarks of NXP B.V.

 $\label{eq:MIFARE} \textbf{MIFARE} - \text{is a trademark of NXP B.V.}$ 

AN14236

All information provided in this document is subject to legal disclaimers.

© 2025 NXP B.V. All rights reserved.

## NTAG X DNA - Antenna design guide

## **Tables**

T 1 4	DIOO :1.1 : 1.0: 5	T	A1.1 '. ('	٠.
1ab. 1.	PICC coil design recommendation5	1ab. 3.	Appreviations	T
Tab. 2.	Theoretical PICC needed bandwidth for a	Tab. 4.	Revision history	13
	data transfer with different data rates 10			

## NTAG X DNA - Antenna design guide

# **Figures**

Fig. 1.	Different coil antenna sizes according to	Fig. 4.	Class 2 antenna example	8
Ū	ISO/IEC 14443-13	Fig. 5.	Resistance trace for determining the	
Fig. 2.	Class 1 antenna examples (with two	· ·	transponder bandwidth	9
	different parameters)6	Fig. 6.	Theoretical needed PICC bandwidth for a	
Fig. 3.	Typical parameters of different class 1 card		data transfer at 424 kB/s	10
	antennas7			

## NTAG X DNA - Antenna design guide

## **Contents**

Introduction	2
How to use this document	2
Card coil design notes for NTAG X DNA	3
	. 3
Card coil area	3
Coil Q-factor	. 3
Measurement of coil Q-factor	. 4
Definition for "loaded" and "unloaded"	
conditions	4
Loaded resonance frequency of the	
transponder	4
Measurement of loaded resonance	
frequency of the transponder	4
NXP recommendation for PICC coil design	. 5
Practical design hints and	
recommendations for the 17 pF chip	
version	. 6
ID1-sized antennas	6
Practical design hints and	
recommendations for the 50 pF chip	
version	. 8
ID ½ sized (class 2) antenna	8
Antenna coil design considerations for	
unloaded and loaded conditions (17 pF IC)	. 9
Quality factor and bandwidth of the	
transponder	9
Required transponder bandwidth for (PICC	
	10
References	12
Revision history	13
Legal information	14
	conditions Loaded resonance frequency of the transponder Measurement of loaded resonance frequency of the transponder NXP recommendation for PICC coil design Practical design hints and recommendations for the 17 pF chip version ID1-sized antennas Practical design hints and recommendations for the 50 pF chip version ID ½ sized (class 2) antenna Antenna coil design considerations for unloaded and loaded conditions (17 pF IC) Quality factor and bandwidth of the transponder

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.