

AN15030

External Hardware Design to Generate CP-PWM Signal Using SIGBRD-HPGP Board

Rev. 1.0 — 18 June 2026

Application note

Document information

Information	Content
Keywords	AN15030, SIGBRD-HPGP board, MCX A154 MCU, electric vehicle (EV), EV charging signal board, sigboard, Home Plug GreenPHY, high-level communication, PLC, ISO 15118, AC charging, DC charging, PWM, control pilot (CP), LIN, LIN-CP
Abstract	This document describes the components required to design external hardware for generating Control Pilot PWM using the SIGBRD-HPGP board. The SIGBRD-HPGP board is an essential component in the EV charger implementation.



1 Introduction

The SIGBRD-HPGP board is an add-on development board used in EV charging solutions. The board has HomePlug GreenPHY (Lumissil CG5317) through SPI and Ethernet host connection interfaces for Control Pilot (CP) connection. In addition, this SIGBRD-HPGP board has an EV side CP-PWM detection circuit only.

This document describes the components required to design external hardware for generating CP-PWM using the SIGBRD-HPGP board. The SIGBRD-HPGP board is an essential component in the EV charger implementation. The SIGBRD-HPGP board also supports the other type of control pilot signal, named 'LIN-CP' for EV supply equipment (EVSE) or EV side of setups.

2 Required hardware

To provide complete the CP functionality, it is required to generate a control pilot signal and detect PWM high-level voltage. The CP signal swings between +12 V to -12 V.

SIGBRD-HPGP has a boost converter to generate +12 V from +5 V. Therefore, to generate -12 V, a charge pump inverter is required inside an external hardware.

To generate and detect CP-PWM, you need an additional circuit shown in [Figure 1](#).

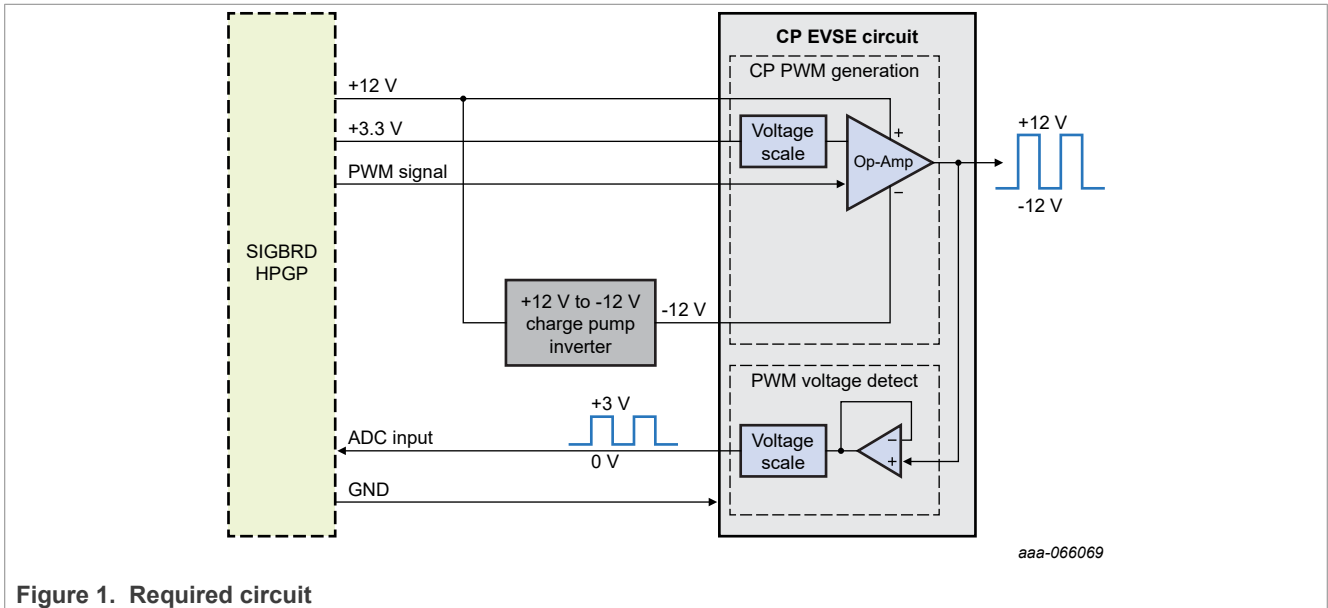


Figure 1. Required circuit

2.1 Charge pump inverter

The CP-PWM signal has a swing between +/-12 V. As the microcontroller MCXA154VFT generates a PWM of 3.3 V level, we need +12 V and -12 V to shift the level of the PWM.

SIGBRD-HPGP only generates +12 V by the boot converter. Therefore, the external charge pump inverted is needed to generate -12 V from +12 V.

[Figure 2](#) shows generation of -12 V from +12 V.

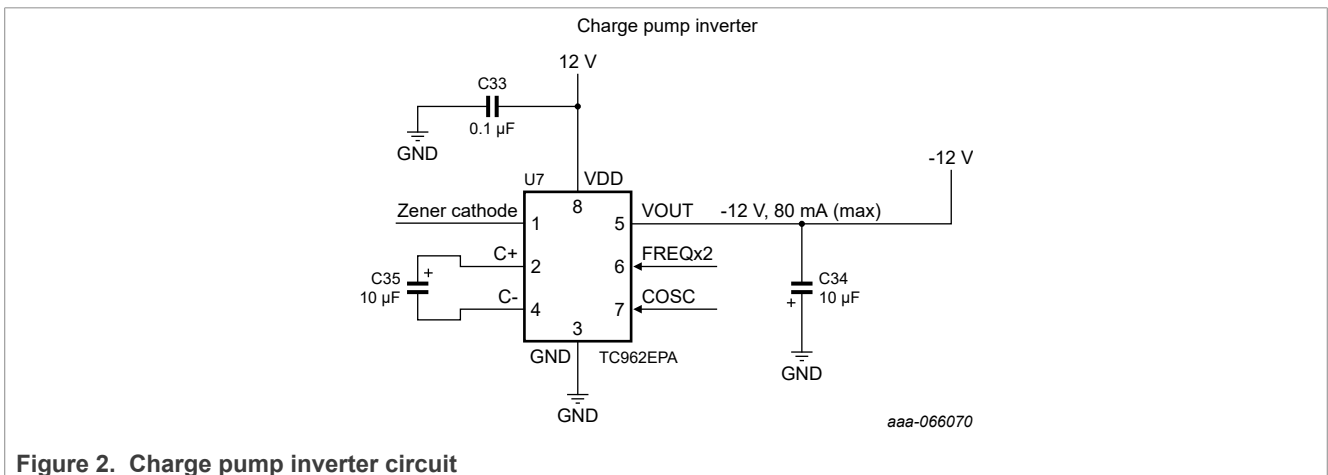


Figure 2. Charge pump inverter circuit

2.2 PWM generation and detection circuit

The CP circuit in the EVSE side has two parts:

- Generation of PWM, and
- Detection of PWM level

Figure 3 shows the generation and detection of CP-PWM signal.

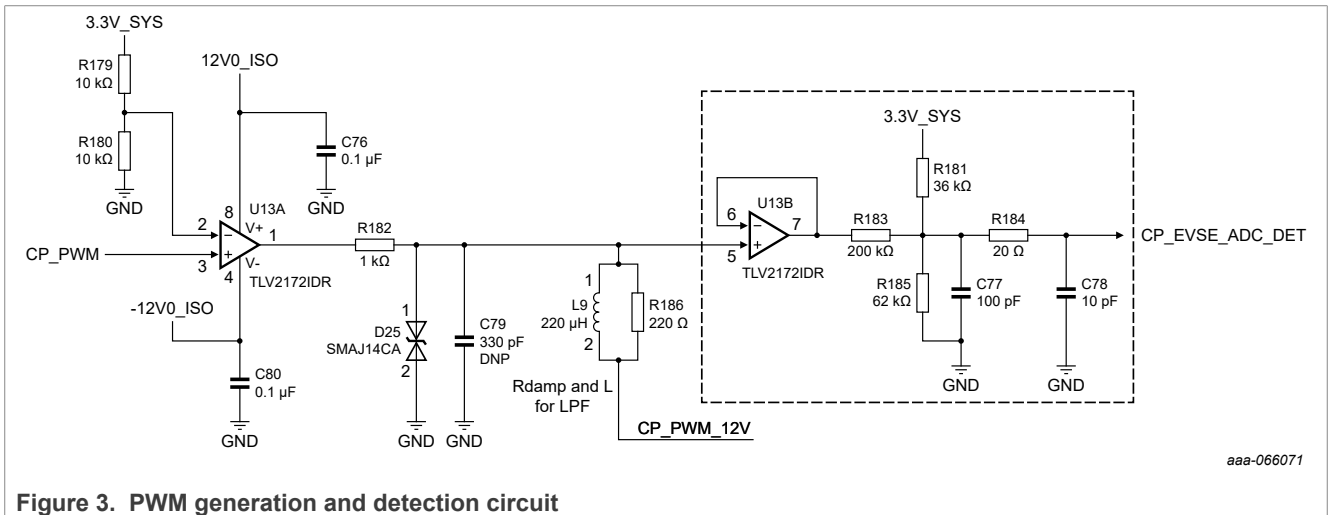


Figure 3. PWM generation and detection circuit

2.2.1 PWM generation circuit

The CP_PWM signal comes from SIGBRD-HPGP. This 3.3 V signal is then amplified to a -12 V to +12 V signal using an Operational Amplifier to generate CP_PWM_12V.

The core of the operation is the TLV2172 Operational Amplifier (U13A), which is configured here as a comparator. The U13A compares the incoming logic-level signal (CP_PWM) at the noninverting input, against a reference voltage created by the R179/R180 divider. The U13A is powered by the bipolar rails (+12V0_ISO and -12V0_ISO). Therefore, it amplifies the 0 V to 3.3 V input voltage into a full-swing ±12 V square wave.

To ensure signal integrity and circuit protection, the output passes through a TVS diode (D25), which clamps high-voltage transients to prevent damage from external surges.

The final stage is a damped low-pass filter formed by inductor L9 and resistor R186. This filter helps to smoothen the high-frequency transitions and manage impedance before the signal exits as CP_PWM_12V to communicate with the Electric Vehicle.

When the CP_PWM_12V signal is connected to an EV, the EV circuit drops the voltage to signal charging.

2.2.2 Detection circuit

In Figure 3, the circuit shown on the right is used to detect the voltage change in the CP_PWM_12V signal. The TLV2172 Operational Amplifier, configured as a voltage follower provides a high-impedance input. The voltage follower buffers the incoming signal without any distortion by the downstream components.

After buffering, the signal enters a biasing and scaling network. In this scaling network, the Resistors R183, R181, and R185 attenuate the voltage and shift it into a positive 0 V to 3.3 V range. This process ensures protecting the ADC from negative or overvoltage conditions.

Finally, the filtering stage consisting of C77, C78, and R184 cleans the signal. This filter circuit removes the high-frequency noise and stabilizes the output for precise digital sampling.

3 External Hardware connections with SIGBRD-HPGP

The external hardware requires 5 input/output connections and a ground shunting. These connections shown in [Table 1](#) can be easily taken out from SIGBRD-HPGP from the jumpers and Arduino connectors.

Table 1. Input/output connection from SIGBRD-HPGP

Signal	Jumper header
+12 V	J40:2
+3.3 V	J29:2
CP_PWM	J31:1
CP_ADC	J31:4
GND	J2:14

Note: The jumpers mentioned in [Table 1](#) are not mandatory and the signals can be taken from the other jumpers/headers as per the design convenience.

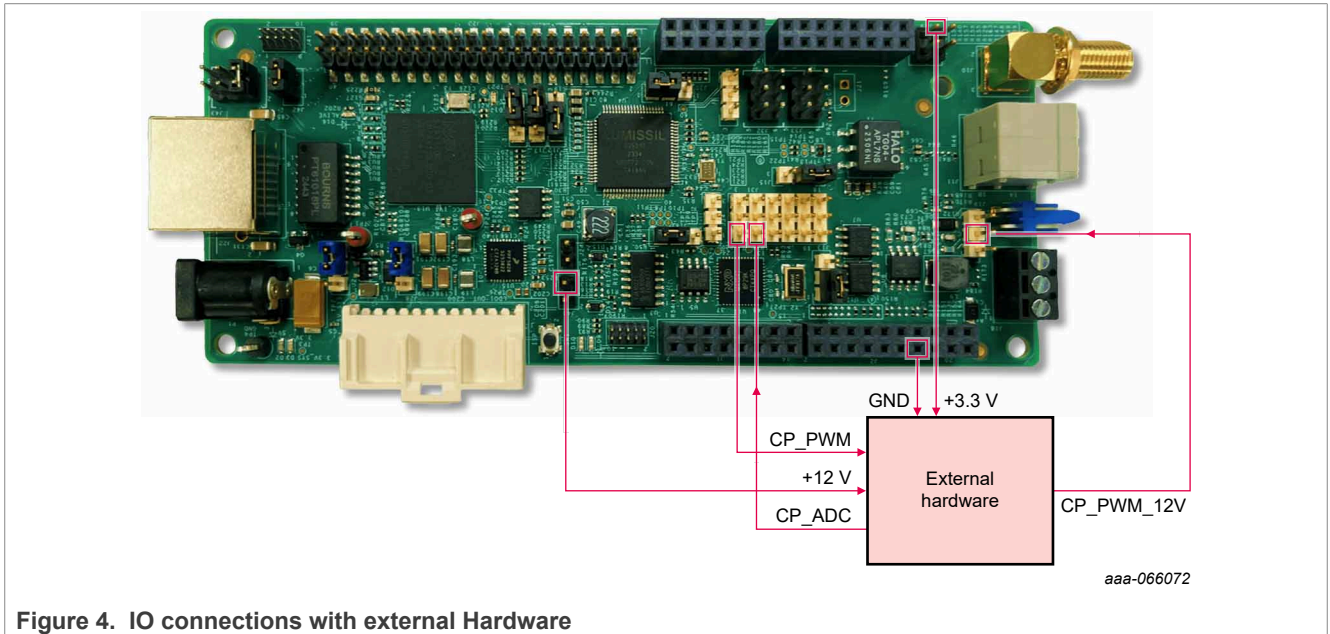


Figure 4. IO connections with external Hardware

4 Acronyms

[Table 2](#) lists the acronyms used in this document.

Table 2. Acronyms

Acronym	Description
ADC	Analog-to-digital converter
CP	Control Pilot
ESP	Enhanced Serial Protocol
EV	Electric Vehicle
EVSE	Electric Vehicle Supply Equipment
GND	Ground
HPGP	Home Plug Green PHY
IP	Internet Protocol or Intellectual Property
IPsec	Internet Protocol Security
LIN	Local Interconnect Network
PWM	Pulse Width Modulation
RDB	Reference Design Board
SIB	Small cell IPsec Backhaul
SIGBRD	Signal Board
SPI	Serial Peripheral Interface
TAP	Test Access Port
TVS	Transient Voltage Suppression

5 Revision history

[Table 3](#) summarizes the revisions to this document.

Table 3. Revision history

Document ID	Release date	Description
AN15030 v.1.0	27 May 2026	Initial public release

Legal information

Definitions

Draft — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Terms and conditions of commercial sale — NXP Semiconductors products are sold subject to the general terms and conditions of commercial sale, as published at <https://www.nxp.com/profile/terms>, unless otherwise agreed in a valid written individual agreement. In case an individual agreement is concluded only the terms and conditions of the respective agreement shall apply. NXP Semiconductors hereby expressly objects to applying the customer's general terms and conditions with regard to the purchase of NXP Semiconductors products by customer.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Suitability for use in non-automotive qualified products — Unless this document expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

HTML publications — An HTML version, if available, of this document is provided as a courtesy. Definitive information is contained in the applicable document in PDF format. If there is a discrepancy between the HTML document and the PDF document, the PDF document has priority.

Translations — A non-English (translated) version of a document, including the legal information in that document, is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Security — Customer understands that all NXP products may be subject to unidentified vulnerabilities or may support established security standards or specifications with known limitations. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately. Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP.

NXP has a Product Security Incident Response Team (PSIRT) (reachable at PSIRT@nxp.com) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

NXP B.V. — NXP B.V. is not an operating company and it does not distribute or sell products.

Trademarks

Notice: All referenced brands, product names, service names, and trademarks are the property of their respective owners.

NXP — wordmark and logo are trademarks of NXP B.V.

External Hardware Design to Generate CP-PWM Signal Using SIGBRD-HPGP Board

Microsoft, Azure, and ThreadX — are trademarks of the Microsoft group of companies.

Contents

1	Introduction	2
2	Required hardware	3
2.1	Charge pump inverter	3
2.2	PWM generation and detection circuit	4
2.2.1	PWM generation circuit	4
2.2.2	Detection circuit	4
3	External Hardware connections with SIGBRD-HPGP	5
4	Acronyms	6
5	Revision history	7
	Legal information	8

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.
