

AN2565/D
Rev. 0.0, 07/2003

Battery Voltage
Detection using the
MC68SZ328

By: Cliff Wong

Contents

- 1 Introduction 1
- 2 Circuit Description..... 1
- 3 Software Description... 2

1 Introduction

In the ADC portion of the ASP module of the MC68SZ328, there is an auxiliary input channel (U-channel) that can be used for low voltage measurement. It is possible to use it to build a battery voltage detection circuit with an accuracy of approximately +/- 20mV at the 3V to 4.2V range.

2 Circuit Description

A small number of external components are required to use the ADC to measure battery voltage. The circuit shown in Figure 1 is composed of three analog switches that are controlled by the programmed GPIO lines of the MC68SZ328. As each input switch is enabled, its value is sampled and then disabled so the next signal can be switched on and measured.

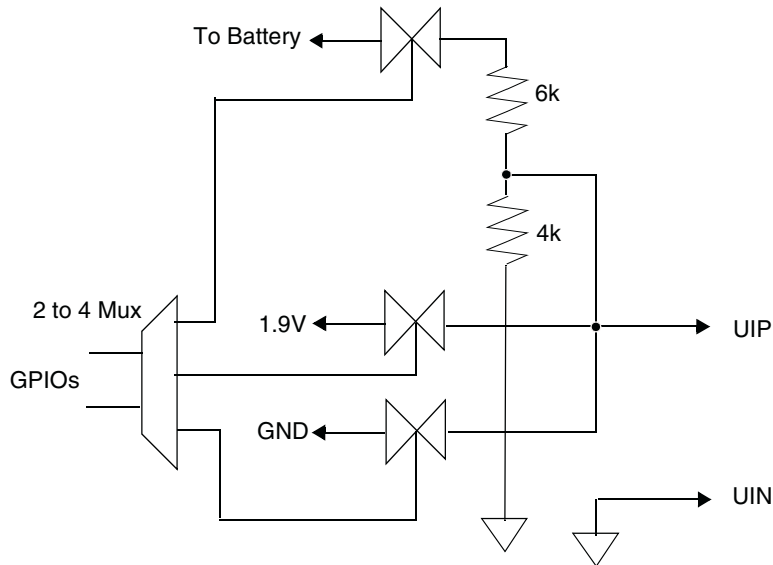


Figure 1. Suggested Battery Voltage Detection Circuit Diagram

There are three signals (battery voltage, 1.9 V reference, and 0V reference or ground) gated to the U-channel by three analog switches; the MC74HC4066 is a good choice for the analog switch.

The 1.9V and 0V source are used to calibrate the reference points for the ADC. From the sample values of these references the software determines the mapping curve of input voltage to output samples.

Since the input to the ADC cannot exceed 1.9V, it cannot be directly connected to the battery. A potential divider circuit should be used to reduce the battery signal presented to the UIP channel. For example, a lithium battery has a voltage range of approximately 3V to 4.2V, so a divider ratio of 3:2 is adequate to develop a voltage less than 1.9V. The total resistance of the divider circuit may range from a few K ohms to 10k ohms. Low tolerance type resistors are recommended for use in the divider, to minimize any error introduced by software.

NOTE:

Because the analog switches are controlled by GPIO lines from the MC68SZ328 using an optional 2-to-4 decoder is recommend to reduce the number of GPIO lines needed to control the three switches.

3 Software Description

This section provides a high-level description of the software algorithm used to determine the battery voltage levels. The process involves two parts: calibration and battery voltage measurement.

- Calibration - Each of the two reference input voltages (1.9 V and 0 V) should be sampled to generate a mean value. It is recommended that all three signals be sampled 12 times to enhance the accuracy of the readings. Each set of 12 FIFO data is used to generate a mean sample value. With the value for 1.9V point and 0V point established, the *slope* and *offset* of the mapping can be calculated. These calculations are based on the assumption that the ADC is linear over the range.
- Battery voltage measurement - Before each the measurement of the battery voltage. the switch controlling the battery voltage should be turned on and then a delay of approximately 100 ms is required for the battery voltage to become stable. Calculating the battery voltage is done by the following equation:

$$\text{Voltage} = ((\text{Sample} - \text{Offset}) / \text{Slope}) * \text{Scaler} \tag{Eqn. 1}$$

Where *offset* is the sample value for 0V input and *scaler* is the potential divider ratio (2.5 in this example)



NOTES

How to Reach Us:

Home Page:
www.freescale.com

E-mail:
support@freescale.com

USA/Europe or Locations Not Listed:
Freescale Semiconductor
Technical Information Center, CH370
1300 N. Alma School Road
Chandler, Arizona 85224
+1-800-521-6274 or +1-480-768-2130
support@freescale.com

Europe, Middle East, and Africa:
Freescale Halbleiter Deutschland GmbH
Technical Information Center
Schatzbogen 7
81829 Muenchen, Germany
+44 1296 380 456 (English)
+46 8 52200080 (English)
+49 89 92103 559 (German)
+33 1 69 35 48 48 (French)
support@freescale.com

Japan:
Freescale Semiconductor Japan Ltd.
Headquarters
ARCO Tower 15F
1-8-1, Shimo-Meguro, Meguro-ku,
Tokyo 153-0064
Japan
0120 191014 or +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:
Freescale Semiconductor Hong Kong Ltd.
Technical Information Center
2 Dai King Street
Tai Po Industrial Estate
Tai Po, N.T., Hong Kong
+800 2666 8080
support.asia@freescale.com

For Literature Requests Only:
Freescale Semiconductor Literature Distribution Center
P.O. Box 5405
Denver, Colorado 80217
1-800-441-2447 or 303-675-2140
Fax: 303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document. Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.



AN2565/D

**For More Information On This Product,
Go to: www.freescale.com**