## **UM11602**

# RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

Rev. 1 — 17 May 2021

**User manual** 

#### **Document information**

| Information | Content   |
|-------------|---|
| Keywords    | 100BASE-T1 Ethernet, media converter, evaluation board, TJA1101B, ARM Cortex-M0+  |
| Abstract    | The RDDRONE-T1ADAPT media converter is intended to be used to evaluate automotive T1 Ethernet. Featuring both a 2-pin 100BASE-T1 Ethernet connector and an RJ45 100BASE-TX connector, the RDDRONE-T1ADAPT allows standard RJ45 and T1 peripherals to communicate over a reliable 2-wire T1 interface. |



## RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

#### **Revision history**

| Rev | Date     | Description     |
|-----|----------|-----------------|
| v.1 | 20210517 | Initial version |

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

#### 1 Introduction

The RDDRONE-T1ADAPT Ethernet adapter board is intended to be used as a platform for evaluating the use of T1 Ethernet in a variety of application areas. This network media converter allows 100BASE-T1 automotive devices and devices with traditional 100BASE-TX incorporating an RJ45 connector to be combined in a single network. This document is the user guide for the RDDRONE-T1ADAPT 100BASE-T1 to RJ45 adapter board. It describes how to use the board to connect a standard 100BASE-TX Ethernet interface to a T1 node or T1 network switch. It also describes how a pair of boards can be used to allow two remote RJ45 nodes to communicate via a reliable two-wire T1 interface by translating 100BASE-TX nodes to 100BASE-T1 and back again to 100BASE-TX.

This release of the adapter board supports 100 Mbit/s links on the RJ45 and T1 connectors. Automatic mode detection is enabled on the T1 connectors, so no further adjustments are needed.

## 2 Finding kit resources and information on the NXP website

NXP Semiconducutors provides online resources for this media converter at <a href="http://www.nxp.com/RDDRONE-T1ADAPT">http://www.nxp.com/RDDRONE-T1ADAPT</a>. A getting started link provides quick-reference information relevant to using the RDDRONE-T1ADAPT along with links to downloadable assets. Additional information can be found at <a href="http://nxp.gitbook.io/rddrone-t1adapt">http://nxp.gitbook.io/rddrone-t1adapt</a>.

## 2.1 Collaborate in the NXP community

The NXP community is for sharing ideas and tips, asking and answering technical questions, and getting input on just about any embedded design topic.

The NXP community is at <a href="https://community.nxp.com">https://community.nxp.com</a>. A dedicated robotics community can be found at <a href="https://community.nxp.com/community/mobilerobotics">https://community.nxp.com/community/mobilerobotics</a>.

#### 3 Kit contents

The RDDRONE-T1ADAPT kit contains:

- · PCB board
- 1 x 2-wire T1 Ethernet cable with JST-GH connector
- 1 x 3-pin (2-wire) power cord with JST-GH connector



Figure 1. T1ADAPT board with supplied T1 and power cables

UM11602

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

## 4 Overview of the RDDRONE-T1ADAPT media converter

The RDDRONE-T1ADAPT Ethernet adapter board is an evaluation platform for automotive two-wire Ethernet (100BASE-T1). It can be used to connect a standard Ethernet device, such as a PC or single-board computer, to a peripheral device with a T1 Ethernet interface. Two RDDRONE-T1ADAPT boards can be used to connect two standard Ethernet devices together via a T1 network. Top and bottom views are shown in Figure 2. Software source code is available on request through NXP sales if the user needs to modify the configuration. However, the board is preprogrammed and designed for plug-and-play operation with no additional software needed.


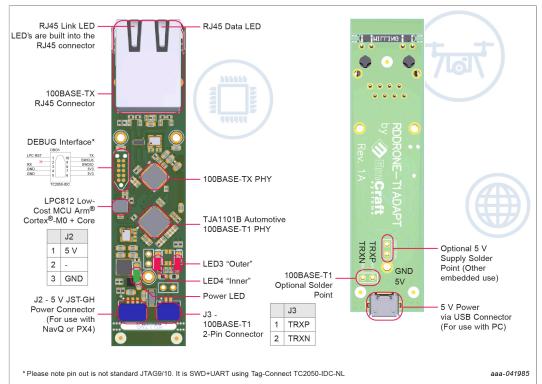


Figure 2. Top and bottom views of the the RDDRONE-T1ADAPT media converter board with main components labeled.

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter
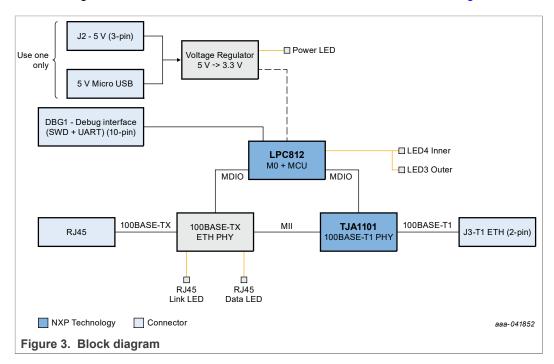
## 4.1 Block diagram


A block diagram of the RDDRONE-T1ADAPT media converter is shown in Figure 3.



#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter
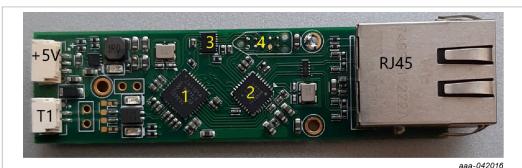
## 4.2 Main components

The main components on the RDDRONE-T1ADAPT board are highlighted in <u>Figure 4</u> and discussed briefly in the following sections.



aaa-042070

Figure 4. Main components on T1ADAPT board

#### 4.2.1 TJA1101B (1)

The TJA1101B 100BASE-T1 automotive Ethernet PHY from NXP Semiconductors is used to support the automotive Ethernet (T1) side of the media converter. The TJA1101B offers 100 Mbit/s transmit and receive capability over an unshielded twisted pair (UTP) cable of up to at least 15 m [1].

#### 4.2.2 100BASE-TX PHY (2)

The 100BASE-TX Ethernet PHY supports the standard Ethernet side of the media converter.

#### 4.2.3 LPC812 (3)


The ARM Cortex-M0+ micro is used to configure the two back-to-back PHYs and to control the master/slave behavior of the TJA1101B [2].


#### 4.2.4 Debug connector (4)

This debug interface, illustrated in Figure 5, can be used to program the device. Since a physical connector is not mounted on the board, a cable such as the TC2050-ID-NL illustrated in Figure 6 can be used to interface with the board via the debug interface. Note that the board is designed for plug-and-play and does not need to be configured for evaluation purposes. The source code is available on request for users that need to adjust the configuration.

**Note:** While the interface accepts standard SWD debugger signals, this is not a standard JTAG/SWD pinout. UART signals have also been included for debugging purposes. A custom wiring or board adapter will need to be configured in order to connect to a traditional JTAG/SWD debugger.
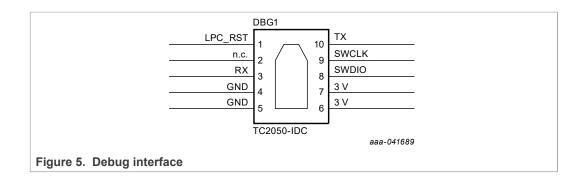
#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter



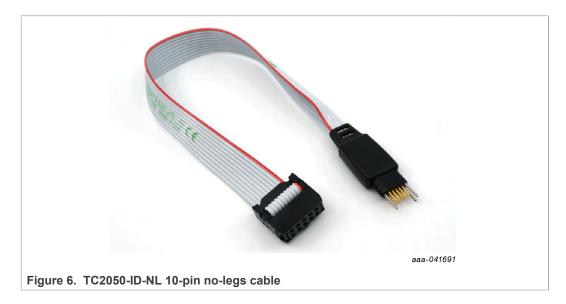

#### 4.2.5 LEDs

A number of status LEDs are provided:

- A green power LED that lights up when power is supplied to the board.
- Two red T1 status LEDs: 'inner' and 'outer' (see <u>Figure 2</u>). A stable T1 connection has been established between the two on-board PHYs when the 'inner' status LED is flashing and the 'outer' status LED is solid on.
- Two green LEDs on the RJ45 connector. An RJ45 connection has been established when the Data status LED is flashing and the Link status LED is solid on.

#### 4.2.6 Connectors

Four physical connectors have been mounted on the board:

- A 3-pin JST-GH power connector
- A 2-pin 100BASE-T1 Ethernet connector
- A standard RJ45 Ethernet connector
- A standard Micro USB connector (mounted on the bottom of the board; see Figure 2)

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

## 5 Power supply

The RDDRONE-T1ADAPT board needs an external 5 V supply. The 5 V supply can be provided by a PC or laptop via the USB connector on the bottom of the board, or via a 3-pin JST-GH power cord. Note that the USB connector is only used to provide the 5 V supply; there is no actual USB data communication. The 3-pin connecter can be used with a single-board computer or NavQ/PX4 device (pin 1 = 5 V; pin 3 = GND).


## 6 System configurations

The RDDRONE-T1ADAPT is designed to interface between standard 100BASE-TX Ethernet and two-wire automotive Ethernet in order to evaluate T1 performance. A number of system configurations are possible.

**Note:** T1 Ethernet is designed to be used with unshielded cable lengths <15 meters.

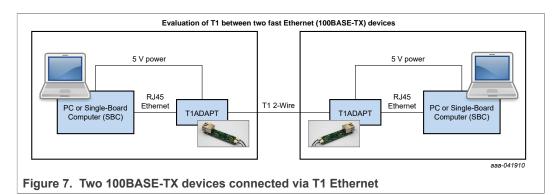
#### 6.1 Evaluating T1 between two 100BASE-TX devices

In <u>Figure 7</u>, a pair of RDDRONE-T1ADAPT boards are used to connect two standard PCs with RJ45 connectors together over a 2-wire T1 network. The adaptors communicate with each other via T1 and the power is supplied by the PCs over USB cables.



#### 6.2 Evaluating communication between a TX and a T1 device

In <u>Figure 8</u>, an RDDRONE-T1ADAPT is used to connect a PC or single-board computer to a T1 peripheral. In this configuration, the power may be supplied through the 3-pin JST-GH connector with 5 V power coming from a pin header or matching connector on the single-board computer.

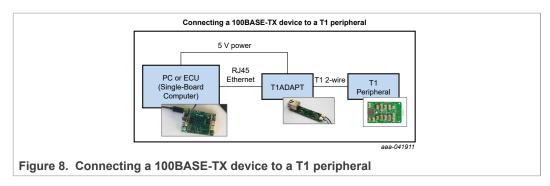


UM11602

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter
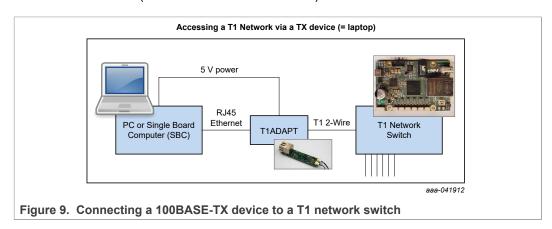
## 6.3 Connecting a 100BASE-TX device to a T1 network switch

In <u>Figure 9</u>, an RDDRONE-T1ADAPT is used to connect a PC or single-board computer to T1 network switch (such as RDDRONE-T1ETH8).



## 7 Operation

Once the RDDRONE T1ADAPT and peripherals have been connected and powered up, the firmware alternates which adapter device is the dominant controller on the T1 bus until a stable connection is established. In the absence of a signal, the firmware resets the PHYs and tries again to establish a link.

#### 8 References

- [1] TJA1101B 100BASE-T1 PHY for automatove Ethernet, <a href="https://www.nxp.com">https://www.nxp.com</a>.
- [2] LPC812 ARM Cortex-M0+ microcontroller, https://www.nxp.com

#### RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

## 9 Legal information

#### 9.1 Definitions

**Draft** — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

#### 9.2 Disclaimers

Limited warranty and liability - Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors. In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory. Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification. Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products. NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or

the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer. In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages. Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Security — Customer understands that all NXP products may be subject to unidentified or documented vulnerabilities. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately. Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP. NXP has a Product Security Incident Response Team (PSIRT) (reachable at PSIRT@nxp.com) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

#### 9.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

NXP — wordmark and logo are trademarks of NXP B.V.

UM11602

## RDDRONE-T1ADAPT 100BASE-T1 to 100BASE-TX media converter

## **Contents**

| 1     | Introduction                             | 3  |
|-------|--|----|
| 2     | Finding kit resources and information on |    |
|       | the NXP website                          | 3  |
| 2.1   | Collaborate in the NXP community         | 3  |
| 3     | Kit contents                             | 3  |
| 4     | Overview of the RDDRONE-T1ADAPT          |    |
|       | media converter                          | 4  |
| 4.1   | Block diagram                            |    |
| 4.2   | Main components                          |    |
| 4.2.1 | TJA1101B (1)                             | 6  |
| 4.2.2 | 100BASE-TX PHY (2)                       | 6  |
| 4.2.3 | LPC812 (3)                               | 6  |
| 4.2.4 | Debug connector (4)                      | 6  |
| 4.2.5 | LEDs                                     | 7  |
| 4.2.6 | Connectors                               | 7  |
| 5     | Power supply                             | 8  |
| 6     | System configurations                    | 8  |
| 6.1   | Evaluating T1 between two 100BASE-TX     |    |
|       | devices                                  | 8  |
| 6.2   | Evaluating communication between a TX    |    |
|       | and a T1 device                          | 8  |
| 6.3   | Connecting a 100BASE-TX device to a T1   |    |
|       | network switch                           | ç  |
| 7     | Operation                                | 9  |
| 8     | References                               |    |
| 9     | Legal information                        | 10 |

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.